
 


BITS ID: _____ NAME: _____ SECTION: _____

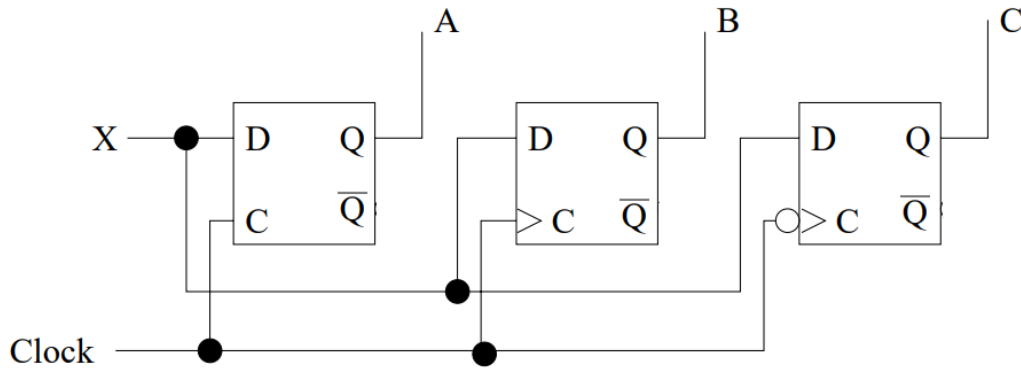Q1 The circuit below has three D flip-flops. Complete the timing diagram by filling in the waveforms for A, B, and C. [8]



Q2 Design and realize a mealy machine using minimum numbers of T flip-flops and logic gates to detect a sequence of 101 in a given input stream. The output goes high on correct detection of last bit of the given sequence. Consider overlapping condition. [8]

- Q3** Draw the logic implementation of $y = f(a, b, c, d)$ for the following Verilog description. [8]
Label all the inputs, output and wires.

```
module gate (y, a, b, c, d)
input a, b, c, d;
output y;
wire w1, w2, w3, w4, w5, w6;
nand n1(w2, a, b, w3);
xor x1 (w1, c, d);
nor n2(w3, a, b, c, w1);
assign w5=w1^w2;
or o1(w6, w1, w2, w4);
and A1(w4, w5, d, a);
assign y=w5 & w6;
end module
```

- Q4** Find the simplest SOP form of the function, $F = X.Y$, where [8]

$$X = ABC\bar{C} + \bar{C}D + \bar{A}C\bar{D} + \bar{B}C\bar{D}$$
$$Y = (A + B + \bar{C} + \bar{D})(\bar{B} + \bar{C} + D)(\bar{A} + C + \bar{D})$$

- Q5** Implement the following function using **only** two 4:1 MUXs (logic gates not allowed). Use A, [8]
B and C as selector lines. $f(A, B, C) = A \oplus B \oplus C$.

- Q1 (a) Draw transistor level implementation of Boolean function Y using CMOS logic family. [20]
Use minimum number of transistors and assume complementary inputs are available.

$$Y = \bar{A}D + \bar{B}(A + \bar{C})$$

- (b) Realize the Boolean function Z using Transmission Gate logic (TG). Assume CMOS inverters and complementary inputs are available.

$$Z = \bar{A} + \bar{B}\bar{C} + \bar{B}C$$

- (c) Analyze and determine the Boolean expression implemented at output V_o using TTL logic as shown in figure 1(a).

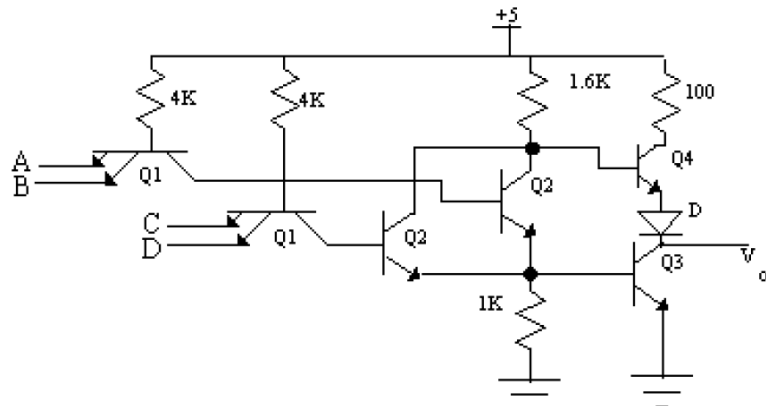


Fig 1(a): TTL Logic Circuit

- Q2 A digital system is to be designed with the following specifications: At power on the circuit is in some initial state T_0 and on next clock edge clears a 4-bit Register (R), 4-bit counter (C) and a flip-flop (E) and goes to next state T_1 . In T_1 register R is loaded with user defined 4-bit data and circuit moves to next state T_2 . In T_2 counter (C) starts counting up. When the C value is equal to R value, E is set on next clock pulse and circuit returns to T_0 . [20]
- Design a ASM chart for the above problem
 - Design Controller using one-hot state assignment
 - Design the datapath required with all status and control signals
- Q3 Design a circuit which has as 4-bit input W [3:0] and 9-bit output X [9:0] where both are treated as 2's complement numbers. Design a logic circuit to make X equal to 6 times W 's value. You may **only** use: • One 8-bit adder (with carry in and carry out) • Three NOT gates • Power and ground. [20]
- Q4 Design a circuit shown in fig 4(a) which generates waveform at output Z . The output Z [20] changes with every clock cycle in the following pattern shown in fig 4(b):

 


Fig 4(a): Digital Circuit

 


Fig 4(b): Pattern

Design the circuit using **only** following components:

- One 4:1 MUX with active high enable.
- One 2:4 Decoder with active high outputs and active high enable.
- Any number of 2-input and 4-input OR gates.
- Two 2-bit binary UP counter with asynchronous clear.
- Two 2-input AND gates.