

Note: Attempt all parts of a question together

Q1 For the given Boolean expression $F(A, B, C, D) = \sum m(0, 1, 3, 6, 8, 10, 12, 14) +$ **[20]**

$\sum d(5, 9, 13, 15)$. Where **A** is MSB and **D** is LSB

- Plot the K-map.
- Identify the Prime Implicants (PI). Express each PI as product form.
- Identify Essential Prime Implicants (EPI). Express each EPI as product form.
- Write down expression for all the possible minimal SOP's of output function **F**.
- Draw the two level circuit diagram of the minimal SOP (any one) using NAND gates. Assume inputs are available in true and compliment forms.

Q2 Realize F_1 and F_2 using a minimum size PLA. Give the size of and draw PLA table. **[10]**

$$F_1(W, X, Y, Z) = \sum m(1, 2, 4, 5, 6, 8, 10, 12, 14)$$

$$F_2(W, X, Y, Z) = \sum m(2, 4, 6, 8, 10, 11, 12, 14, 15)$$

Q3 a) Realize the following function **F** using only ONE 4:1 multiplexer with active high enable. Only true (uncomplimeted) inputs are available. **[20]**

$$F(W, X, Y, Z) = \sum m(3, 4, 5, 7, 10, 14) + \sum d(1, 6, 15)$$

Q4 Design and realize a 2-bit magnitude comparator circuit as shown in figure 1, using **only** minimum numbers of Multiplexers (4:1) and Decoders (2:4). Assume enable of both components are active high and outputs of decoders are active high. **[20]**

 


Figure 1: 2-bit Magnitude Comparator

Q5 Design a single Mealy machine to detect the sequence 1001 and 010 in a given input stream. The circuit has one serial input **X** and one output **Z**. The output goes HIGH on correct detection of last bit of any of the given sequences. Consider the overlapping condition. Realize the Mealy machine using minimum number of D flip-flops and external logic gates. Draw a Mealy state diagram and Mealy state table. Assume unused states (if any) as don't care. **[20]**