

6. While designing a new PE (programmable element) structure, designers have to make a choice between using a small size LUT with additional elements or a large size LUT. Assume that your manager has asked you to design a combinational 3-input, 3-output PE structure, which is optimal for implementation of a 4-bit incremter circuit (Assume $A(A_3A_2A_1A_0)$ as input and $O(O_3O_2O_1O_0)$ as output. If input is 0000, incremter output will be 0001)

Initially, you have come up with two different designs. Figure 6(a) shows first design with one 2-input, 3-output LUT and two 2:1 multiplexers. Figure 6 (b) shows second design with just one 3-input, 3-output LUT and no additional elements.

To determine which PE design is better, implement a 4-bit incremter optimally using

(a) least number of PEs, when PE structure is as shown in Figure 6(a)

(b) least number of PEs, when PE structure is as shown in Figure 6(b)

Comment on advantages and disadvantages of both the PE designs with respect to the implementation of 4-bit incremter. [12M]

(Full marks will be awarded only if the designs are optimal and use least number of PEs. Partial marks may be given for correct implementations which are not optimal and/or use more PEs. For each circuit implementation, show the interconnection between PEs clearly and for each LUT, instead of truth table, mention the logic function implemented by outputs as a function of inputs)

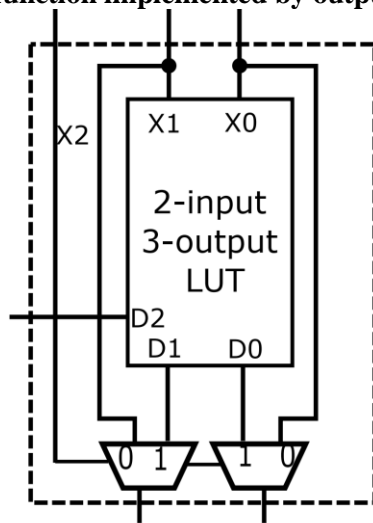


Figure 6(a): PE Design 1

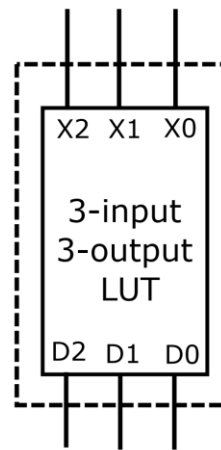


Figure 6(b): PE Design 2