


**BITS ID:**

**Name:**


- Q1 Realize the Boolean expression using the minimum number of Transmission Gates (TGs). [5]  
 $F(A, B, C, D) = \sum m(0, 4, 5, 6, 8, 9) + d(10, 11, 12, 13, 14, 15)$ . True and compliment inputs are available.

- Q2 For the following sequential circuit, construct the state table. [5]

State	Present State		Input $X$	Output $Z$	Flip-flop Input		Next State $Q_2^+ Q_1^+$
	$Q_2$	$Q_1$			$J_2 K_2$	$J_1 K_1$	
$S_0$	0	0	0				
	0	0	1				
$S_1$	0	1	0				
	0	1	1				
$S_2$	1	0	0				
	1	0	1				
$S_3$	1	1	0				
	1	1	1				

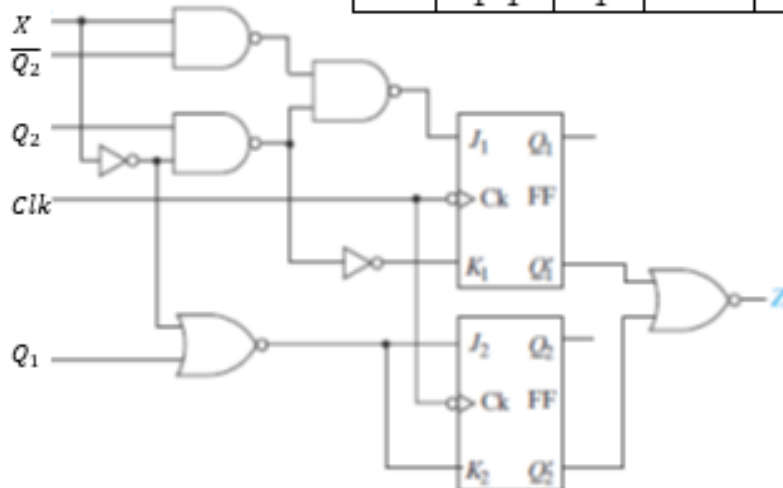

 Q3 A 4-bit shift register is shown in the figure below. It is clocked, and with each clock pulse, the pattern gets shifted by a one-bit position to the right. [5]



Assume that the initial value of the shift registers as 1001. Write the content of the shift registers after the following clock pulses:

	1	0	0	1
After 1 <sup>st</sup> clock pulse				
After 3 <sup>rd</sup> clock pulse				
After 5 <sup>th</sup> clock pulse				
After 7 <sup>th</sup> clock pulse				

To what values should the shift register be initialized so that the pattern (1001) occurs after the first clock pulse:


--	--	--	--

Q4 Use the following table to perform the multiplication of two numbers, M (multiplicand) and Q (multiplier), using the booth's algorithm. [5]

Assume  $M = -12$  and  $Q = 8$ .


A	Q	Q <sub>-1</sub>	Count	Command
00000	01000	0	-	Initialization

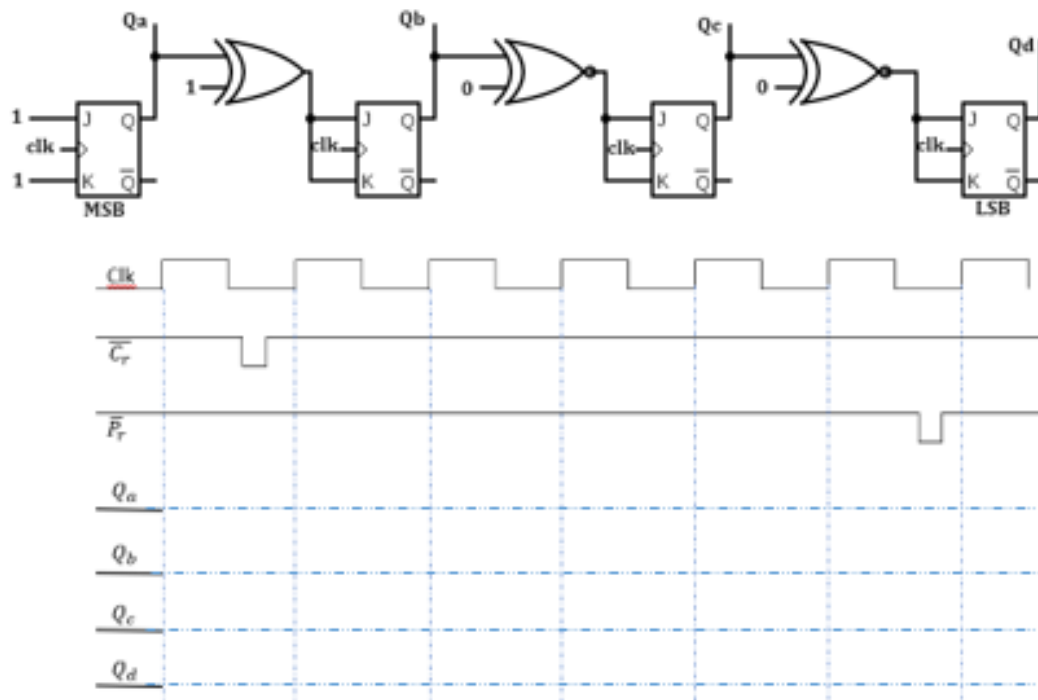Q5 Draw the waveform corresponding to the circuit below; assume that preset and clear (both active low) of all the flipflops are commonly connected to " $\overline{P_r}$ " and " $\overline{C_r}$ " respectively. Clock is common to all flipflop. [5]



Q6 A full subtractor has three input (X, Y, Bin) and two output (D, Bout). Realize the Bout expression using minimum number of CMOS transistors. True and compliment inputs are available. [5]

 Q7 Identify the logic operation the given circuit performs on input A and input B. Also, complete the following table with respect to the state of the respective transistor (ON or OFF) for the various input combinations. [5]



An operation performed is:

Input A	Input B	Q3	Q4	Q5	Q6	Output Z
0	0					
0	1					
1	0					
1	1					

Q8 Complete the partial truth table for the given Verilog code: [5]

```

module Mini (
  input P, Q,
  output X, Y
);
  assign X = P ^ Q;
  assign Y = ~P & Q;
endmodule

module Top (
  input P, Q, R,
  output Q1, Q2
);
  wire A, B, C;

  Mini L0(P, Q, A, B);
  Mini L1(A, R, Q1, C);

  assign Q2 = B | C;
endmodule

```

P	Q	R	Q1	Q2
1	1	1		
0	0	1		
0	1	1		
1	0	0		
0	1	0		