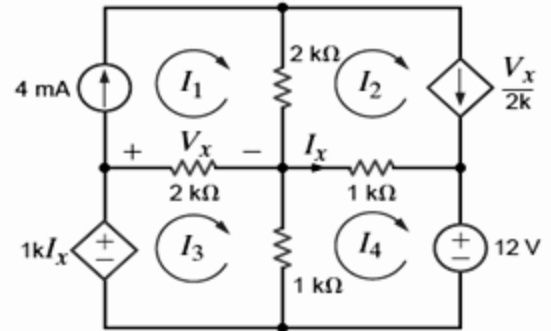


Note: Attempt all the parts of a question in sequence.

Make neat solutions showing all the necessary steps.


Q1. For the circuit shown in figure, find the loop currents $I_1, I_2, I_3,$ and I_4 using mesh analysis. Also determine the power supplied by independent voltage source. [25]



Q2. Two inductive coils (coil means: resistance in series with inductance) A and B are in parallel across a 100V, 50 Hz supply. Coil A takes 12 A at 0.9 power factor and the total current for both the coils is 20 A at 0.8 power factor. All current and voltages values are in rms. Determine:

- The equivalent resistance and reactance of the coils combination.
- The individual resistances and reactances of both coils.
- The value of capacitance to be connected in parallel with the coils to improve the overall power factor to 0.95 lagging. [30]

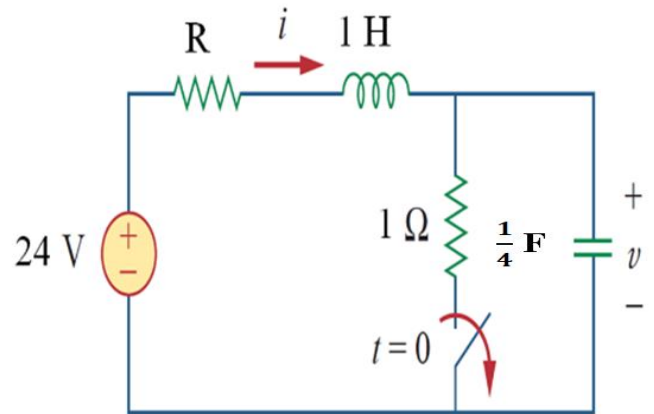Q3. For the circuit shown in figure, assume that the switch has been kept closed for a long time and it is opened at $t=0$. Determine, $v(t)$ and $i(t)$ for $t \geq 0s$ and sketch these functions, when $R=1\Omega$. [25]



Q4(a). For the circuit shown in Fig 4(a) find the following:

- Find the expression of resonant frequency in terms of circuit elements.
- If $R_1 = 1 \Omega, R_2 = 10 \Omega, L = 10 \text{ mH}, C = 18\mu\text{F}$, determine the value of resonant frequency.
- Find Z_{in} at the resonance for the values as given in (ii).

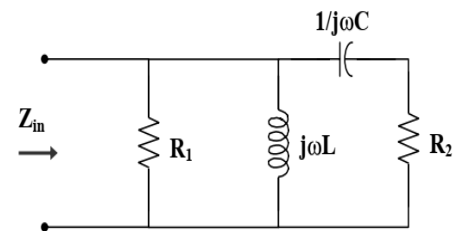


Fig 4(a)

- Now, refer Fig 4(b), derive the transfer function V_o/V_{in} in terms of circuit elements and identify the type of filter. Also determine the half power frequencies. [25]

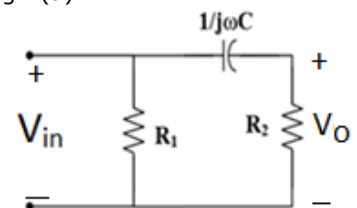


Fig 4(b)