

**Time: 90 min.**

**Max. Marks = 80**

**Date: 13-3-2022 (9-10:30 am)**

**Unless given specifically**

Take --  $V_{DD}/V_{CC} = 4\text{ V}$ ,

**For NMOS device**  $\mu_n C_{ox} = 140\ \mu\text{A}/\text{V}^2$ ,  $V_{Tn} = 0.7\text{ V}$ ,  $\lambda = 0.1\text{ V}^{-1}$ ,  $\gamma = 0.45\ \sqrt{\text{V}}$ ,  $C_{ox} = 0.38\text{ pF}/\mu\text{m}^2$

**For PMOS device**  $\mu_p C_{ox} = 40\ \mu\text{A}/\text{V}^2$ ,  $V_{Tp} = -0.8\text{ V}$ ,  $\lambda = 0.1\text{ V}^{-1}$ ,  $\gamma = 0.4\ \sqrt{\text{V}}$ ,  $C_{ox} = 0.38\text{ pF}/\mu\text{m}^2$

**For NPN/ PNP**  $\beta = 100$ ,  $|V_{BE}| = 0.7\text{ V}$ , and  $V_t = 25\text{ mV}$ ,  $\alpha = 1$ ,  $I_S = 10^{-12}\text{ A}$ ,  $V_A = 100\text{ V}$ ,  $V_{ce,sat} = 0.2\text{ V}$

**NOTE:**

If not specified in the question, -----


- Ignore  $\gamma$ ,  $\lambda$  in the drain current equation. Assume matched components wherever required
- Specify your assumptions. Justify your answers. Unless specified, assume all MOSFETs are biased in the saturation region. Label your sketches properly. All symbols have usual meaning.
- The body (B) terminals of all the PMOSFETs are connected to  $V_{DD}$ , NMOSFETs are connected to the ground.

**Q1. (a)** Consider the Circuit shown in **Fig. 1**.

$V_{DD} = 5\text{ V}$ ,  $R_D = 5\text{ k}\Omega$ ,  $V_{GSQ} = 2\text{ V}$ ,  $\mu_n C_{ox} (W/L) = 0.5$

$\text{mA}/\text{V}^2$ ,  $V_{tn} = 0.8\text{ V}$ ,  $\lambda \approx 0$ .

 - I. Calculate the quiescent values  $I_{DQ}$  and  $V_{DSQ}$ .
- II. Determine the low-frequency small signal voltage gain ( $v_o/v_i$ ).
- III. If  $v_i = 0.1 \sin \omega t\text{ V}$ , sketch and label the  $i_o$  and  $V_o$  waveforms properly with respect to time.




**Q1. (b)** For the circuit given below in **Fig. 2**:

$\beta = 100$ ,  $R_1 = 200\text{ k}\Omega$ ,  $R_2 = 200\text{ k}\Omega$ ,  $R_{E1} = 240\ \Omega$ ,  $R_{E2} = 20\text{ k}\Omega$ ,  $R_C = 2\text{ k}\Omega$ ,  $V_{BE(ON)} = 0.7\text{ V}$ ,


$V_A = \infty$ ,  $V_{Thermal} = 0.025\text{ V}$

 - I. Identify the circuit topology.
- II. Calculate the  $I_{CQ}$  and  $V_{CEQ}$ .
- III. Find small signal parameters  $g_m$  and  $r_{\pi}$ .
- IV. Draw and label the small signal model and calculate the low-frequency voltage gain ( $V_{out}/V_s$ ).
- V. How will the  $I_{CQ}$  change for the given circuit if the value of  $R_{E1} = R_{E2} = 0$  in the circuit? Comment on the operating region of the amplifier after the above change.



**[22 Marks]**

**Q2.** Consider the 2-port network representation of a unilateral system shown in **Fig. 3**.

 

**Fig. 3**

Given ----

- When  $S_1$  closed and  $S_2$  closed:  $V_1 = 0.5V$ ,  $I_1 = 10\mu A$  and  $I_2 = 1mA$
- When  $S_1$  open and  $S_2$  open:  $I_2 = 1mA$  and  $V_2 = 5V$ .


- Find the **h-parameter** matrix. Also, Sketch and label the **h-parameter** model of the network.
- Find the **z-parameter** matrix. Also, sketch and label the **z-parameter** model of the network.
- If a signal source  $V_i = 0.5V$  is connected to port 1 of the **z-parameter** model and a load resistance of  $25k\Omega$  is connected to port 2 of the model. Now, calculate the following in **dB**; voltage gain ( $V_{out}/V_i$ ), current gain ( $I_o/I_i$ ) and Power gain.

[18 Marks]

**Q3.** Consider the circuit of **Fig. 4**. Ignore the body bias effect (Perform intuitive analysis)

Given: MOSFET:  $\lambda=0.1V^{-1}$ ,  $V_{tn}=1V$ ,  $\mu_n C_{ox} = 100\mu A/V^2$ ,  $V_{ov} = 0.2V$

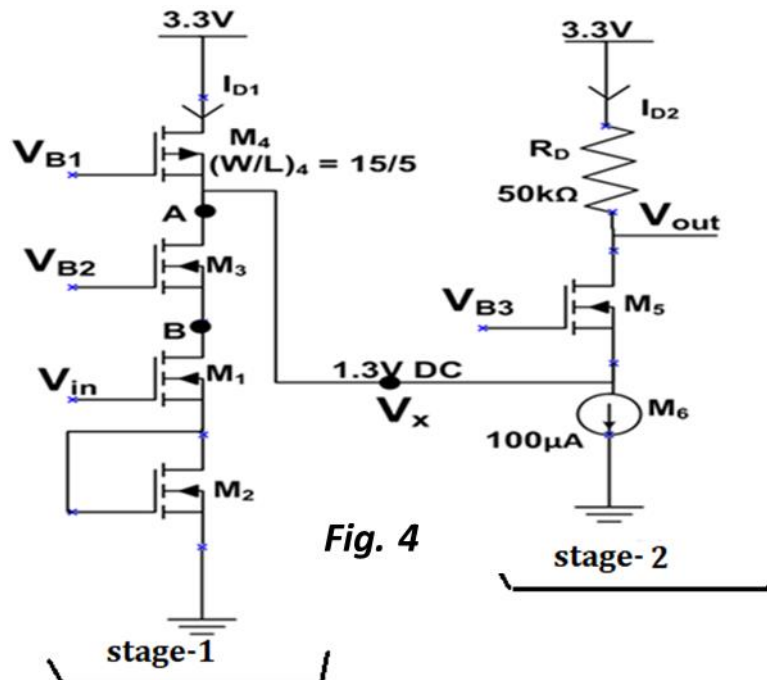BJT:  $V_{BEon} = 0.6V$ ,  $V_A= 100V$  and  $V_{CEsat} = 0.2V$


 


**Fig. 4**

- I. Identify the topology of **stage 1** and **stage 2**.
- II. Calculate the current  $I_{D1}$ .
- III. Calculate the voltage swing at nodes  $V_x$  and  $V_{out}$ .
- IV. Sketch and label the **small signal model**.
- V. Calculate the  $G_m$  and  $R_{out}$  of **Stage-1**. Hence, find the gain  $V_x/V_{in}$  and  $V_{out}/V_x$ . (Hint: Consider loading effect of stage 2 in calculations)
- VI. Assume, node  $V_x$  is **connected to node B**. Now, calculate  $G_m$  and  $R_{out}$  of **first stage** (Hint: Consider loading effect of stage 2 in calculations) [25 Marks]

**Q4.** Circuit shown in **Fig. 5(a)** is used to bias circuit shown in **Fig. 5(b)**, and generate voltages  $V_{B1}$ ,  $V_{B2}$ ,  $V_{B3}$ , using MOSFET transistors. Assume all the transistors are operating in active region.

- Given that the total power consumption of **Fig 5(a)** and **Fig. 5(b)** together is  $7500 \mu W$
- Assume  $|V_T| = 1V$ ,  $V_{ov} = 0.2V$  for all the transistors.

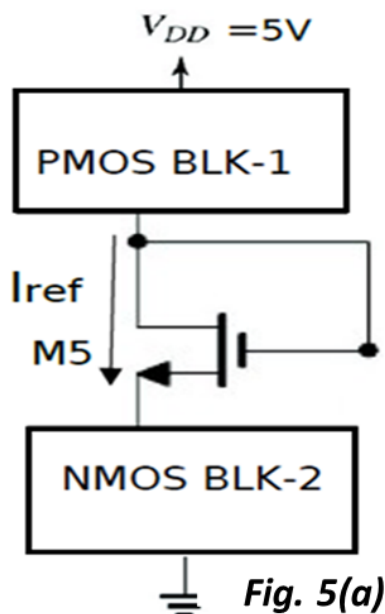

- I. Determine the value of  $I_{REF}$  current.
- II. Now, sketch the schematic of **NMOS block (BLK2)** in **Fig. 5(a)**.
- III. Draw the circuit (schematic) of **PMOS block (BLK1)** in **Fig. 5(a)**. Hence, draw the complete circuit of **Fig. 5(b)** including biasing circuit.
- IV. Now, for **Fig. 5(b)**, compute **DC** values of voltages  $V_{B1}$ ,  $V_{B2}$  and  $V_{B3}$
- V. Determine the value of  $V_{GS}$  of transistor **M5** shown in **Fig. 5(a)**. [15 Marks]

-----XXX-----