

**Birla Institute of Technology and Science, Pilani**

**Comprehensive exam (close book), second semester 2016-17**

**Power Systems (EEE F312)**

**Max. Marks – 120**

**Duration- 180 minutes**

**May 12, 2017**

**Instructions:** Write your assumptions clearly with justifications; Doubts are a part of questions. So, no clarification please!

- Q1. For the network shown in fig.Q1, a balanced three-phase resistor is fed by a balanced line (with mutual coupling between phases). Find positive, negative and zero sequence currents and hence the currents in the three phases **a, b** and **c** for  $V_a = V$ ;  $V_b = 0$ ;  $V_c = 0$ . [10, 10]

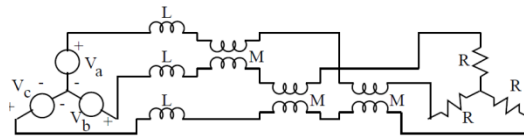


Fig.Q1

- Q2. One-line diagram of a power system is shown fig.Q2. Find the per unit fault current (point of fault is shown) in the lines for (a) single Line-Ground fault and (b) Double Line-Ground fault. [Clearly draw the network in both cases using positive, negative and zero sequence networks for current calculation]. {The system parameters are: System Base Voltage = 138kV; System Base Power = 100MVA; Transformer  $T_1$  Leakage Reactance = 0.1 pu; Transformer  $T_2$  Leakage Reactance = 0.1 pu; Line  $L_1$  Positive and Negative Sequence Reactance =  $j(0.05)$ pu; Line  $L_1$  Zero Sequence Impedance =  $j0.1$ pu; Line  $L_2$  Positive and Negative Sequence Reactance =  $j(0.02)$ pu; Line  $L_2$  Zero Sequence Impedance =  $j0.1$ pu}. [20, 20]

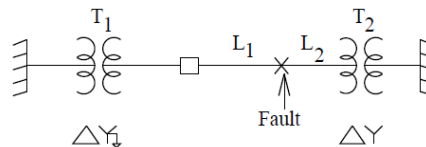


Fig.Q2

- Q3. A synchronous generator of reactance  $1.20 \text{ pu}$  is connected to an infinite bus bar through transformers and a line of total reactance of  $0.60 \text{ pu}$ . The generator no load voltage is  $1.20 \text{ pu}$  and its inertia constant is  $H = 4 \text{ MW-s/MVA}$ . The resistance and machine damping is assumed to be negligible. The system frequency is 50 Hz. Calculate the frequency of natural oscillations if the generator is loaded to (a) 50% and (b) 80% of its power limit. [15]
- Q4. A power deficient area receives 50MW over a tie line from another area. The maximum steady state capacity of the tie line is 100MW. Find the allowable sudden load that can be switched on without loss of stability. [15]
- Q5. A three phase feeder having a resistance of 3 ohm and a reactance of 10 ohm supplies a load of 2 MW at  $0.85 \text{ pf}$  lag. The receiving end voltage is maintained at 11 kV by means of a static condenser drawing 2.1 MVAR from the line. Calculate the sending end voltage and power factor. What is the regulation and efficiency of the feeder? [15]
- Q6. Incremental fuel costs in rupees per MWh for a plant consisting of two units are:  $dC_1/dP_{G1} = 0.20P_{G1} + 40.0$  and  $dC_2/dP_{G2} = 0.25P_{G2} + 30.0$ . Assume that both the units are operating at all the times, and load varies from 40 MW to 250 MW, and the maximum and minimum loads on each units are to be 125 MW and 20 MW respectively. What is the load sharing of each unit for a plant output of 40 MW and 175 MW. [15]