

BIRLA INSTITUTE OF TECHNOLOGY AND SCIENCE, PILANI
FIRST SEMESTER 2022-23
EEE G581 RF AND MICROWAVE ENGINEERING
COMPREHENSIVE EXAMINATION (OPEN BOOK)

Date: 22-12-2022

Duration: 180 Minutes

Marks: 60

Instruction: Answer all questions. Unclear / illegible answers will not be evaluated

Q1) A double-stub tuner uses shunt stubs to match a load admittance $Y_L / Y_0 = 0.4 + j1.2$. The stubs are separated by $3\lambda/8$ and stub-1 is placed at the load. Choose stub-1 as SC stub and stub-2 as OC stub. Obtain the stub lengths (both solutions) in units of wavelength. Use **Smith chart-1** for the design. [15 M]

Q2) A low-pass filter must be designed and realized for 50Ω impedance, 5 GHz cut-off frequency and 0.25 dB equi-ripple passband. Corresponding prototype element values are given below,

$$g_0=1, g_1=1.3034, g_2=1.1463, g_3=1.3034, g_4=1$$

Start the lumped model with an inductor. Next realize the filter using all-shunt commensurate length ($\lambda/8$) microstrip lines. Present the design evolution using *neat and clear* diagrams showing *every detail* of element values, impedances, lengths etc. at every design stage. (Need not calculate the microstrip line widths) [20 M]

Q3) A GaAs HBT has the following S-matrix measured at 5 GHz, and 50Ω reference impedance.

$$S = \begin{bmatrix} 0.75 \angle -140^\circ & 0.07 \angle +65^\circ \\ 3.00 \angle +85^\circ & 0.55 \angle -40^\circ \end{bmatrix}$$

(a) If an amplifier is built using the above device, could it become potentially unstable?

(b) *Neatly shade* the unstable (or stable) region of the amplifier in **Smith chart-2**.

(c) If the amplifier is connected to a source with $Z_S=25 \Omega$ and load with $Z_L=100 \Omega$, calculate the transducer power gain in dB.

(d) Compare the above gain with the gain calculated under unilateral assumption. [25 M]

***** END *****