BIRLA INSTITUTE OF TECHNOLOGY AND SCIENCE, PILANI FIRST SEMESTER 2023-24 EEE G581 RF AND MICROWAVE ENGINEERING MID SEMESTER TEST (CLOSED BOOK)

Date: 11-10-2023

Duration: 90 Minutes

Max marks: 40

[8]

Instruction: Answer all questions

Q1) A 4-port network is described by the S-matrix given below. Port 2 is matched. A matched lossless transmission line of length $\lambda/3$ is connected between ports 3 and 4. Find port1 to port2 transmission coefficient (T₂₁) [10]

[S] =	[.0.4/-45°	0	0	0.5/45° -	1
	0	0.7∠-45°	0.6/45°	0	L
	0	0.6∠45°	0.72-45°	0	L
	0.2∠50°	0	0	0.4∠-45°	

Q2) An RF source with 75 Ω output impedance is connected to a planar device having 33 Ω input impedance. Propose an *appropriate* impedance matching section between the two at 2.4 GHz. Find the design parameters of the matching section that can be realised using microstrip technology with W/d > 2. Use a substrate of dielectric constant 3 and thickness 1.58 mm. [10]

Q3) A 1-port device is represented by an input impedance of 80 Ω resistance in series with 10 nH inductance. A 50 Ω lossless transmission line excites the device at 800 MHz. Use *only* the Smith chart to solve the following.

(i) Find the VSWR and reflection coefficient for the load [6]

(ii) Design a short-circuited series stub to match the load to the line if VSWR =1 is required at the junction. The stub should be as close to the load as possible [6]

(iii) Repeat (ii) if VSWR=2 is required at the junction.

Attach separate Smith charts for (ii) and (iii)

$$\begin{split} \epsilon_{e} &= \frac{\epsilon_{r} + 1}{2} + \frac{\epsilon_{r} - 1}{2} \frac{1}{\sqrt{1 + 12d/W}} & \frac{W}{d} = \begin{cases} \frac{8e^{A}}{e^{2A} - 2} & \text{for } W/d \leq 2\\ \frac{2}{\pi} \left[B - 1 - \ln(2B - 1) + \frac{\epsilon_{r} - 1}{2\epsilon_{r}} \left\{ \ln(B - 1) + 0.39 - \frac{0.61}{\epsilon_{r}} \right\} \right] & \text{for } W/d > 2, \end{split}$$

$$A &= \frac{Z_{0}}{60} \sqrt{\frac{\epsilon_{r} + 1}{2}} + \frac{\epsilon_{r} - 1}{\epsilon_{r} + 1} \left(0.23 + \frac{0.11}{\epsilon_{r}} \right)$$

$$B &= \frac{377\pi}{2Z_{0}\sqrt{\epsilon_{r}}}, \end{split}$$