

BIRLA INSTITUTE OF TECHNOLOGY AND SCIENCE, PILANI
FIRST SEMESTER 2023-24
EEE G581 RF AND MICROWAVE ENGINEERING
COMPREHENSIVE EXAMINATION (OPEN BOOK)

Date: 12-12-2023

Duration: 180 Minutes

Marks: 65

Instruction: Answer all questions. Unclear or randomly presented answers will not be evaluated

Q1) A microstrip transmission line is fabricated on Polyimide substrate which is available with ϵ_r in the range of 2.3-13.4. For maximum bandwidth operation, what value of ϵ_r should be selected? Find the maximum bandwidth if the substrate thickness is 2 mm. [5 M]

Q2) VNA measurement of the reflection coefficient is performed for a standard coaxial cable at a frequency of 2.45 GHz. The VNA reads $0.7\angle -75^\circ$ when the cable termination is *MATCHED* while it reads $0.3\angle 175^\circ$ when the termination is changed to *SHORT*. Obtain the S-matrix for the cable. [5 M]

Q3) A load impedance of $60-j45 \Omega$ needs to be transformed to $Z_{in}=120+j22.5 \Omega$. Design an open-circuited single-stub tuner to be added in shunt with the line to achieve the transformation. The design should result in the shortest stub location. Assume $Z_0=75 \Omega$ for all transmission lines used. Use **Smith chart-I** for the design. [15 M]

Q4) Test the amplifier circuit for stability whose S-matrix is given below. Shade the stable region on **Smith chart-II** with clear marking of all parameters [20 M]

$$S = \begin{bmatrix} 0.70\angle -70^\circ & 0.20\angle -10^\circ \\ 5.50\angle +85^\circ & 0.7\angle -45^\circ \end{bmatrix}$$

Q5) A BJT amplifier circuit has scattering parameters, $S = \begin{bmatrix} 0.55\angle -140^\circ & 0.00 \\ 2.00\angle +85^\circ & 0.75\angle -40^\circ \end{bmatrix}$.

(a) The source circuit of this amplifier is designed to have a gain 1 dB less than its maximum value. What is the maximum transducer gain of this amplifier in dB ?

(b) Draw the constant gain (G_S) circle on **Smith chart-III**

(c) Assume $\Gamma_s = 0.40\angle 94^\circ$ is selected from the gain circle as the design value. Draw the corresponding constant noise figure circle with $R_F=0.36$ and $\angle \Gamma_{opt}=56^\circ$ on the same chart and hence find C_F [20 M]

***** END *****