

BIRLA INSTITUTE OF TECHNOLOGY AND SCIENCE, PILANI
First Semester 2023-2024
Mid-semester exam (Open book)
INSTR F311-Electronic Instruments and Instrumentation Technology

Time: 90 Minutes


Max Marks:60

Date 11.10.2023

- 1) (a) A PMMC meter with $50\ \Omega$ internal resistance can draw a maximum 100 mA current. The same meter is used to design a multi-range DC voltmeter to measure voltage ranges: 0-10 V, 0-20 V, and 0-40 V respectively as shown in **Figure 1**. You have given a pool of 1 W power rating resistors having resistance values in multiples of 10 ($10\ \Omega$, $20\ \Omega$, $30\ \Omega$, $40\ \Omega$, $50\ \Omega$ ----- $390\ \Omega$, $400\ \Omega$).
- (i) The theoretical values of R_1 , R_2 and R_3 to design a multi-range voltmeter with given ranges.
- (ii) To realize this multi-range DC voltmeter practically, which resistors one should choose from the given pool of 1 W resistors for R_1 , R_2 , and R_3 ? Justify your answer.
- (iii) If the pointer deflects 90° in all three voltage ranges, calculate the input voltage in each case assuming the range of deflection scale is 0-150°.


[3+3+2]

Figure 1

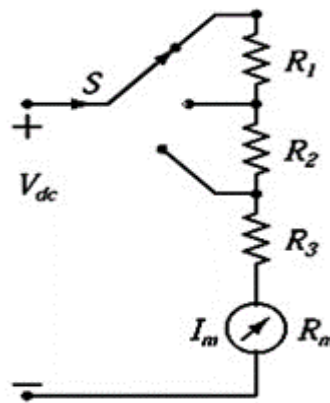

- 1) (b) A PMMC meter with $900\ \Omega$ coil resistance and a maximum meter current of $75\ \mu\text{A}$ is to be used with a full wave rectifier circuit as an AC voltmeter along with a shunt resistance connected in parallel to the meter. Silicon diodes are used with a forward voltage drop of 0.7 and a minimum peak diode forward current of $80\ \mu\text{A}$ when the meter indicates 0.4FSD (full-scale deflection). Draw the circuit diagram showing the values of shunt and multiplier resistance that are required for the AC voltmeter to indicate 100V rms at its full scale.
- [8]
- 2) (a) A galvanometer has a coil wound on a rectangular aluminum former of resistivity $27 \times 10^{-9}\ \Omega\text{m}$. The length and width of the former are 40 mm and 25 mm respectively. The former moves in a uniform magnetic flux density of 0.15 T against a controlling torque produced by a spring of constant $15 \times 10^{-6}\ \text{Nm/rad}$. The moment of inertia of the moving system is found to be $60 \times 10^{-9}\ \text{Kgm}^2$. Determine the cross-sectional area of the aluminum former if it is to provide critical damping by neglecting the other sources of damping in the galvanometer.
- [9]
- 2) (b) An electro-dynamometer wattmeter has a current coil of $0.2\ \Omega$ resistance with a reactance of $0.08\ \Omega$. The potential coil is assumed to be purely resistive and the total potential coil circuit has a resistance of $7500\ \Omega$. Calculate the percentage errors in the indicated power by the wattmeter for the below two configurations of current and potential coils, if the load takes 12 A current at a voltage of 250 V with a power factor of 0.6.
- (i) when the current coil is on the load side.
- (ii) when the potential coil is on the load side.
- [4+4]

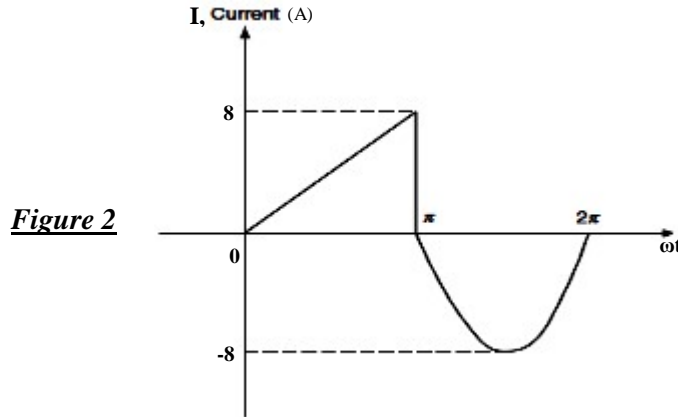- 3) (a) Calculate the reading that would be observed on a moving coil ammeter and moving iron ammeter when it is measuring current in a circuit whose waveform for one cycle is shown in **Figure 2**. [9]



- 3) (b) A shunt-type ohm-meter with a battery voltage of V volts shown in **Figure 3** uses an electronic voltmeter with a full-scale reading of $V/4$ volts, which measures the voltage across the unknown resistance R_x as E_v between the terminals A & B respectively.
- (i) What should be the relation between R_1 and R_2 to get a full-scale reading in the electronic voltmeter?
- (ii) Determine the unknown resistance R_x in terms of R_1 and R_2 , if the electronic voltmeter indicates one-fourth of its full-scale reading. [2+4]

- 4) (a) Draw a practical emitter follower voltmeter circuit specifying all the missing component values by utilizing the data given below:
 Supply voltages $\pm 8V$, $I_3 = I_2 = 3.07 \text{ mA}$, $h_{FE} = 100$, $I_4 = 2.53 \text{ mA}$, $R_4 = R_6 = 3 \text{ k}\Omega$, $R_m = 1 \text{ k}\Omega$, and meter gives full-scale deflection at $100 \mu\text{A}$ when $E = 1 \text{ V}$ (consider V_{BE} for the transistors as $0.7V$). [8]

- 4) (b) An AC electronic voltmeter circuit shown in **Figure 4** has $R_1 = 10 \text{ k}\Omega$, $R_2 = 3.2 \text{ k}\Omega$, $R_3 = 6.8 \text{ k}\Omega$, and $R_m = 0.5 \text{ k}\Omega$ respectively. The meter gives full-scale deflection (FSD) for $200 \mu\text{A}$. Calculate
- (i) rms input voltage E for meter FSD.
- (ii) rms output voltage V_{out} for 0.5FSD. [2+2]

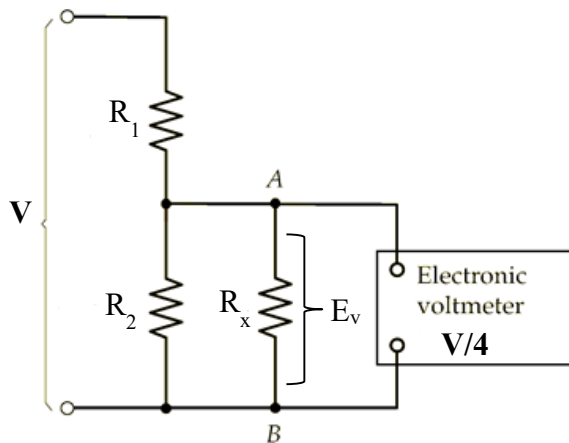


Figure 3

