

**Department of EEE, BITS PILANI K. K. BIRLA GOA CAMPUS**

**Mid-Semester Question Paper – Analog IC Design (MEL G 632)**

Date: 18-03-2023

Time: 11:00 hours to 12:30 hours

Duration: 90 minutes



Closed Book

Full-Marks: 25

Attempt All Questions. Please use the Table given at the end to select appropriate values wherever they are not given in the question.



- (a) Assume that  $V_{DD}$  varies from 4V to 6V and  $V_{SS} = 0$  in Fig. 1(a). Assume due to process variation,  $k'_n/p$ ,  $V_{thn}$  and  $|V_{thp}|$  also vary and can be estimated by  $k'_n = 110 \pm 10\%$ ,  $k'_p = 50 \pm 10\%$ ,  $V_{thn} = |V_{thp}| = (0.7 \pm 0.15)$  V. If  $I_{SS} = 100 \mu A$ ,  $(\frac{W}{L})_{1,2} = 5$ ,  $(\frac{W}{L})_{3,4} = 1$  and drop across  $V_{DS-M5} = 0.2$  V. Include worst case variation to calculate input common-mode range. Ignore L-diffusion, body effect and channel length modulation.

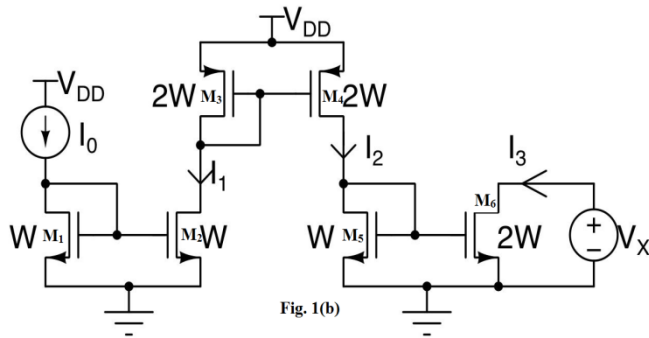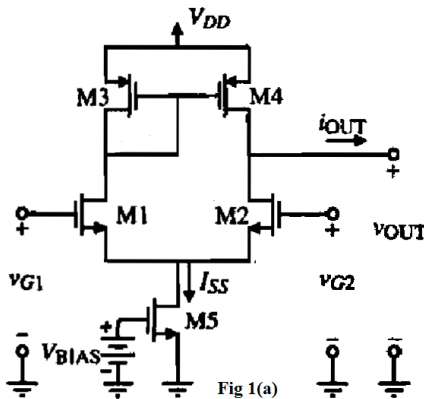- (b) In the Fig. 1(b), what is the value of  $I_1$ ,  $I_2$  and  $I_3$ ? Given  $\lambda = 0.1V^{-1}$ , threshold voltage = 0.5 V and overdrive = 0.2 V for all the devices, while  $V_{DD} = 1.8$  V. Further  $V_x = 0.3V$  and  $I_0 = 1$  mA. All the devices have same channel length. Assume  $\lambda V_{DS} \ll 1$  for all the devices and neglect 2<sup>nd</sup> and higher order terms of  $\lambda$ .



4(=1+1+2)+3×2 = 10-marks

- Design the circuit of Fig. 2 for a voltage gain of  $|20|$  and a power budget of 1 mW with  $V_{DD} = 1.8$  V. Assume  $M_1$  operates at the edge of saturation if the input common-mode level is 1 V. Also,  $\mu_n C_{ox} = 2\mu_p C_{ox} = 100 \mu A/V^2$ ,  $V_{THN} = 0.5$  V,  $V_{THP} = -0.4$  V,  $\lambda_p = 2\lambda_n = 0.1V^{-1}$ . Take  $L_{geo} = 1\mu m$  (neglect L-diffusion).

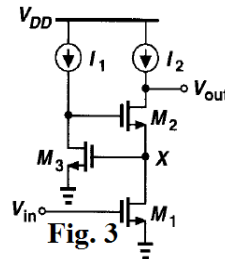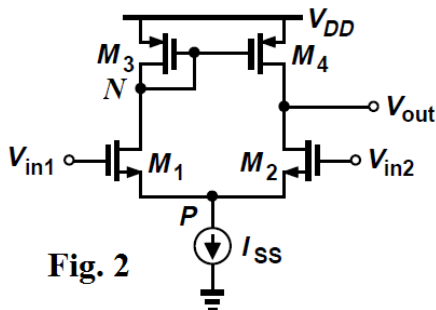

3+3= 6-marks

3. If  $I_1 = 1\text{mA}$ ,  $I_2 = 750\ \mu\text{A}$ ,  $2 \times \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_{1,2} = \frac{5\ \mu\text{m}}{0.5\ \mu\text{m}}$  in Fig. 3, find  $R_{\text{out}}$  and voltage gain without using any approximation. Consider channel length modulation, L-diffusion and assume  $g_{\text{mb}} = 0.1g_m$ .

3+2= 5-marks

4. Find RMS noise voltage of a  $1/f$  noise source with  $\bar{V}_n(f)^2 = (50\ \text{nV})^2/f$ , over the range of frequency from 1 Hz to 100 MHz. What is the RMS noise voltage if the lower limit of the frequency is reduced to 10 nHz? Give your answer in  $\mu\text{V}$  in both cases.

2+2= 4-marks

Table of Values

Parameters	$V_{\text{Th}}(\text{V})$	$\gamma (\sqrt{V})$	$\phi_f(\text{V})$	$L_D (\text{m})$	$\lambda(\text{V}^{-1})$ for $L_{\text{Geo}}=0.5\ \mu\text{m}$	$k'_{n/p} = \mu_{n/p}C_{\text{OX}}(\text{A/V}^2)$
NMOS	0.7	0.5	0.9	$0.08 \times 10^{-6}$	0.1	$134.26 \times 10^{-6}$
PMOS	-0.8	0.4	0.8	$0.09 \times 10^{-6}$	0.2	$38.36 \times 10^{-6}$
Common	$n_i = 1.45 \times 10^{10}\text{cm}^{-3}$ , $q = 1.6 \times 10^{-19}\text{C}$ ; $k = 1.38 \times 10^{-23}\frac{\text{J}}{\text{K}}$ ; $V_{DD} = V_{CK} = 3.0\text{V}$ ; $V_{SS} = 0\text{V}$ ; $\beta_{\text{NPN}} = 150$ , $\beta_{\text{PNP}} = 100$ , Room Temperature = $27^\circ\text{C}$ ; $\epsilon_{\text{Si}} = 11.68$ ; $\epsilon_{\text{SiO}_2} = 3.6$ ; $\epsilon_0 = 8.85 \times 10^{-12}\frac{\text{F}}{\text{m}}$ ; $C_{\text{GDO}_{\text{NMOS}}} = 0.4 \times 10^{-9}\frac{\text{F}}{\text{m}}$ ; $C_{\text{ox}} = 6.9\ \text{fF}/\mu\text{m}^2$ for $t_{\text{ox}} = 50\ \text{\AA}$					

Table of Equations (You might have seen in a distant galaxy...)

1.	$I_D = \frac{1}{2}\mu_{n/p}C_{\text{OX}}\left(\frac{W}{L}\right)(V_{\text{GS}} - V_T)^2$ ; $I_D = \frac{1}{2}\mu_{n/p}C_{\text{OX}}\left(\frac{W}{L}\right)(V_{\text{GS}} - V_T)^2(1 + \lambda V_{\text{DS}})$ when channel length is included
2.	$\phi_0 = \frac{kT}{q} \ln\left(\frac{N_D N_A}{n_i^2}\right)$
3.	$Q_{\text{B0}} = -\left(1 - \frac{\Delta L_S + \Delta L_D}{2L}\right)\sqrt{2q\epsilon_{\text{Si}}N_A 2\Phi_F }$
4.	$C_{\text{jo}} = \sqrt{\frac{q\epsilon_{\text{Si}}}{2}\left(\frac{N_D N_A}{N_D + N_A}\right)\frac{1}{\Phi_0}}$
5.	$\Delta V_{\text{T0}} = \frac{1}{C_{\text{ox}}}\sqrt{2q\epsilon_{\text{Si}}N_A 2\Phi_F }\frac{x_j}{2L}\left[\left(\sqrt{1 + \frac{2x_{\text{ds}}}{x_j}} - 1\right) + \left(\sqrt{1 + \frac{2x_{\text{dd}}}{x_j}} - 1\right)\right]$
6.	$x_d = \sqrt{\frac{q\epsilon_{\text{Si}}}{2}\left(\frac{N_D N_A}{N_D + N_A}\right)(\Phi_0 - V)}$